

Chapter 31 *Electromagnetic Oscillations and Alternating Current*

2. According to $U = (1/2)LI^2 = (1/2)Q^2/C$, the current amplitude is

$$I = \frac{Q}{\sqrt{LC}} = \frac{3.00 \times 10^{-6}}{\sqrt{(1.10 \times 10^{-3})(4.00 \times 10^{-6})}} = 4.52 \times 10^{-2} \text{ (A)}.$$

6. (a) The angular frequency is

$$\omega = \sqrt{\frac{k}{m}} = \sqrt{\frac{F/x}{m}} = \sqrt{\frac{8.0}{(2.0 \times 10^{-3})(0.50)}} = 89 \text{ (rad/s)}.$$

(b) The period is $1/f$ and $f = \omega/2\pi$. Therefore,

$$T = 2\pi/\omega = 2\pi/(89 \text{ rad/s}) = 7.0 \times 10^{-2} \text{ s}.$$

(c) From $\omega = 1/(LC)^{1/2}$, we obtain

$$C = \frac{1}{\omega^2 L} = \frac{1}{(89)^2 (5.0)} = 2.5 \times 10^{-5} \text{ (F)}.$$

9. The time required is $t = T/4$, where the period is given by $T = 2\pi/\omega = 2\pi(LC)^{1/2}$. Consequently,

$$t_{1/4} = \frac{2\pi\sqrt{LC}}{4} = \frac{2\pi\sqrt{(0.050)(4.0 \times 10^{-6})}}{4} = 7.0 \times 10^{-4} \text{ (s)}.$$

10. We find the inductance from $f = \omega/2\pi$ and $\omega = 1/(LC)^{1/2}$, $L = 1/(4\pi^2 f^2 C) = 1/[4\pi^2 (10 \times 10^3)^2 (6.7 \times 10^{-6})] = 3.8 \times 10^{-5} \text{ (H)}$.

28. (a) We use $I = \epsilon_m/X_C = \epsilon_m \omega_d C = 2\pi f_d C \epsilon_m$:

$$I = 2\pi(1.00 \times 10^3)(1.50 \times 10^{-6})(30.0) = 0.283 \text{ (A)}.$$

(b) $I = 2\pi(8.00 \times 10^3)(1.50 \times 10^{-6})(30.0) = 2.26 \text{ (A)}$.

29. (a) The current amplitude I is given by $I = V_L/X_L$, where $X_L = \omega_d L = 2\pi f_d L$. Since the circuit contains only the inductor and a sinusoidal generator, $V_L = \epsilon_m$. Therefore,

$$I = \frac{\epsilon_m}{2\pi f_d L} = \frac{30.0}{2\pi(1.00 \times 10^3)(50.0 \times 10^{-3})} = 95.5 \text{ (mA)}.$$

(b) The frequency is now eight times larger than in part (a), so the inductive reactance X_L is eight times larger and the current is one-eighth as much. The current is now

$$I = (0.0955 \text{ A})/8 = 0.0119 \text{ A} = 11.9 \text{ mA}.$$

39. (a) The capacitive reactance is

$$X_C = \frac{1}{2\pi f_d C} = \frac{1}{2\pi(60.0)(70.0 \times 10^{-6})} = 37.9 \text{ (}\Omega\text{)}.$$

The inductive reactance 86.7Ω is unchanged. The new impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(200)^2 + (37.9 - 86.7)^2} = 206 \text{ (}\Omega\text{)}.$$

(b) The phase angle is

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{86.7 - 37.9}{200}\right) = 13.7^\circ.$$

(c) The current amplitude is

$$I = \epsilon_m / Z = 36.0 \text{ V} / 206 \Omega = 0.175 \text{ A}.$$

(d) We first find the voltage amplitudes across the circuit elements:

$$V_R = IR = (0.175 \text{ A})(200 \Omega) = 35.0 \text{ V},$$

$$V_L = IX_L = (0.175 \text{ A})(86.7 \Omega) = 15.2 \text{ V},$$

$$V_C = IX_C = (0.175 \text{ A})(37.9 \Omega) = 6.62 \text{ V}.$$

Note that $X_L > X_C$, so that ϵ_m leads I . The phasor diagram is drawn to scale below. (Figure)

41. The resistance of the coil is related to the reactances and the phase constant by Eq. 31-65. Thus,

$$\frac{X_L - X_C}{R} = \frac{\omega_d L - 1/\omega_d C}{R} = \tan \phi,$$

which we solve for R :

$$R = (\omega_d L - \frac{1}{\omega_d C}) \tan^{-1} \phi = 89 \Omega.$$

43. (a) Yes, the voltage amplitude across the inductor can be much larger than the amplitude of the generator emf. (b) The amplitude of the voltage across the inductor in an RLC series circuit is given by $V_L = IX_L = I\omega_d L$. At resonance, the driving angular frequency equals the natural angular frequency:

$\omega_d = \omega = 1/\sqrt{LC}$. For the given circuit

$$X_L = \frac{L}{\sqrt{LC}} = \frac{1.0 \text{ H}}{\sqrt{(1.0 \text{ H})(1.0 \times 10^{-6} \text{ F})}} = 1000 \Omega.$$

At resonance the capacitive reactance has this same value, and the impedance reduces simply: $Z = R$. Consequently,

$$I_{\text{resonance}} = \epsilon_m/R = 10 \text{ V} / 10\Omega = 1.0 \text{ A}.$$

The voltage amplitude across the inductor is therefore $V_L = IX_L = (1.0 \text{ A})(1000 \Omega) = 1.0 \times 10^3 \text{ V}$, which is much larger than the amplitude of the generator emf.

59. $R = 15.0 \Omega$, $C = 4.70 \mu\text{F}$, $L = 25.0 \text{ mH}$, $f = 550 \text{ Hz}$, and $\epsilon_m = 75.0 \text{ V}$. (a) The rms current is

$$I_{\text{rms}} = 2.586 \text{ A} \approx 2.59 \text{ A}$$

$$= \frac{\epsilon_{\text{rms}}}{Z} = \frac{\epsilon_{\text{rms}}}{\sqrt{R^2 + (2\pi fL - 1/2\pi fC)^2}}.$$

(b) The rms voltage across R is

$$V_{ab} = I_{\text{rms}} R = (2.586)(15.0) = 38.8 \text{ V}.$$

(c) The rms voltage across C is

$$V_{bc} = I_{\text{rms}} X_C = \frac{I_{\text{rms}}}{2\pi fC} = 159.2 \text{ V} \approx 159 \text{ V}.$$

(d) The rms voltage across L is

$$V_{cd} = I_{\text{rms}} X_L = 2\pi I_{\text{rms}} f L = 223.4 \text{ V} \approx 223 \text{ V}.$$

(e) The rms voltage across C and L together is

$$V_{bd} = |V_{bc} - V_{cd}| = |159.2 \text{ V} - 223.4 \text{ V}| = 64.2 \text{ V}.$$

(f) The rms voltage across R , C and L together is

$$V_{ad} = \sqrt{V_{ab}^2 + V_{bd}^2} = \sqrt{(38.8 \text{ V})^2 + (64.2 \text{ V})^2} = 75.0 \text{ V}$$

(g) For R , $P_R = \frac{V_{ab}^2}{R} = \frac{(38.8 \text{ V})^2}{15.0 \Omega} = 100 \text{ W}$.

(h) No energy dissipation in C .

(i) No energy dissipation in L .

重點整理—第 31 章 電磁振盪與交流電

(同學如有需要,請自行複習第 15 章—力學振盪)

LC 能量轉移 於 LC 振盪電路中, 能量於電容器之電場與電感器之磁場間轉移(此類似於木塊 m -彈簧 k 振盪), 兩種形式能量瞬間值

$$U_E = \frac{q^2}{2C} \quad (vs \ U_{sp} = \frac{1}{2} kx^2), \quad U_B = \frac{1}{2} Li^2 \quad (vs \ K = \frac{1}{2} mv^2),$$

式中 q 為電容器中瞬時電荷, 而 i 為通過電感器之瞬時電流. 總能量 $U (=U_E + U_B)$ 仍然固定。

($m-k$ vs LC : $k \rightarrow C^{-1}$, $m \rightarrow L$, $x \rightarrow q$, $dx/dt \rightarrow dq/dt$)

LC 電荷與電流振盪 能量守恆原裡導得 LC 振盪微分方程式 $L \frac{d^2q}{dt^2} + \frac{1}{C}q = 0$ (LC 振盪).

其解為 $q = Q \cos(\omega t + \phi)$ (電荷), $i = -\omega Q \sin(\omega t + \phi)$ (電流), 式中 Q 為電荷振幅, 而振盪角頻率為 $\omega = 1/\sqrt{LC}$; 相位常數 ϕ 由系統初始條件決定。

交流電; 強迫振盪 RLC 串聯電路可藉外交流電動勢, $\varepsilon = \varepsilon_m \sin(\omega_d t)$, 使其以驅使角頻率 ω_d 作強迫振盪, 電動勢驅使的電流, $i = I \sin(\omega_d t - \phi)$, 式中 I 及 ϕ 為電流之振幅及相位常數。

單一電路元件 跨過元件之電位差與電流之振幅及相位關係: (a) 對電阻器, $V_R = IR$, 兩者同相; (b) 對電容器, $V_C = IX_C$, 而 $X_C = 1/\omega_d C$ 為容抗, 電流超前電位差 90° 或 $\pi/2$ 相位 ($\phi = -90^\circ$); (c) 對電感器, $V_L = IX_L$, 而 $X_L = \omega_d L$ 為感抗, 電流落後電位差 90° 相位 ($\phi = 90^\circ$)。

Note 電容器與電感器之交流頻率響應截然不同, 低頻時, 電容器如同斷路, 而電感器如同短路; 高頻時, 電容器如同短路, 而電感器如同斷路。

RLC 串聯電路 對具外電動勢, $\varepsilon = \varepsilon_m \sin(\omega_d t)$, 之 RLC 串聯電路, (穩定態) 電流為 $i = I \sin(\omega_d t - \phi)$, 電流振幅 $I = \frac{\varepsilon_m}{Z}$, $Z = \sqrt{R^2 + (X_L - X_C)^2}$ 為阻抗, $X_L = \omega_d L$, $X_C = 1/\omega_d C$, 而相位常數 $\tan \phi = \frac{X_L - X_C}{R}$.

Note 利用容抗感抗或阻抗, 使各元件之電壓與電流之關係如同遵守歐姆定律般。

共振 RLC 串聯電路被正弦變化的外電動勢驅使時, 當驅使頻率 ω_d 等於自然角頻率 ω 時, 其電流振幅最大, 即在共振; 共振時, 電抗等於感抗, $X_C = X_L$, 而電流與電動勢同相, $\phi = 0$, $I = \varepsilon_m/R$ 。

電功率 在 RLC 串聯電路, 發電機之平均功率 P_{av} 等於電阻器上熱能產生速率

$$P_{av} = I_{rms}^2 R = \varepsilon_{rms} I_{rms} \cos \phi,$$

上式中下標 rms 表示平方-平均-平方根(方均根), 方均根與最大量(振幅)之關係為 $I_{rms} = I/\sqrt{2}$, $V_{rms} = V/\sqrt{2}$, $\varepsilon_{rms} = \varepsilon_m/\sqrt{2}$, $\cos \phi$ 項稱為電路功率因子。

變壓器 理想變壓器就是匝數 N_p 之原線圈及匝數 N_s 之副線圈纏繞的軟鐵芯. 若原線圈與交流發電機連通, 原電壓與副電壓的關係為

$$V_s / N_s = V_p / N_p \text{ or } V_s = V_p (N_s / N_p) \quad (\text{電壓變換}).$$

流經線圈之電流的關係為

$$I_s N_s = I_p N_p \text{ or } I_s = I_p (N_p / N_s) \quad (\text{電流變換}).$$

再者從發電機觀之, 副線圈之等效電阻為

$R_{eq} = (N_p/N_s)^2 R$, 式中 R 為副電路之電阻負載; 比值 N_p/N_s 稱為變壓器匝數比。

太陽爆發如何癱瘓電力網系統?

electromagnetic oscillation 電磁振盪; resonance 共振; alternating current (ac) 交流電; direct current (dc) 直流電; reactance 電抗; capacitive reactance 容抗, 電容性電抗; inductive reactance 感抗, 電感性電抗; impedance; 阻抗; power factor 功率因子; root-mean-square (rms) 方均根; transformer 變壓器; primary/ secondary coil 原/副線圈; turn ratio 匝數比; iron core 鐵芯; (electric) generator 發電機; power grid 電力網; malfunction 發生故障; overtax 超載, 負擔過度;

S1. 台電提供日常生活用電, 電壓 $V_{rms} = 110 \text{ V or } 220 \text{ V}$, 而頻率 $f = 60 \text{ Hz}$.

S2. 某量 $a(t)$ 與時間關係呈正弦變化 $A \cos(\omega t + \phi)$, 則其方均根與振幅關係可藉 $\frac{1}{T} \int_0^T dt \cos^2(\omega t + \phi) = \frac{1}{2}$ 以得.

●備忘錄●