

Chapter 18 (Bueche & Jerde) *Direct-Current Circuits*

P06 $r = 2.0 \text{ m}$, $v = 1.0 \times 10^5 \text{ m/s}$ & $q = 1.8 \mu\text{C}$. $\Delta t = 2\pi r/v = 1.26 \times 10^{-4} \text{ s}$, $I = \Delta q/\Delta t = 0.0143 \text{ A}$.

P19 $\rho = 1.70 \times 10^{-8} \Omega \cdot \text{m}$, $d = 1.024 \text{ mm}$ & $\ell = 20 \text{ m}$: (a) $R = \rho L/A = 0.413 \Omega$; (b) $V = IR = 4.95 \text{ V}$.

P22 $\rho = 10^{-6} \Omega \cdot \text{m}$, diameter $d = 1.0 \text{ mm}$. $R = \rho L/A$, $L = RA/\rho = \pi(d/2)^2 R/\rho = 19.7 \text{ m}$.

P24 $\Delta R = R_0 \alpha \Delta T$, $\Delta R/R_0 = 0.00450 \times (36.0 - 15.0) = 9.45\%$.

P27 $P = 100 \text{ W}$, $V = 120 \text{ V}$, $P = IV = V^2/R$: (a) $I = P/V = 0.833 \text{ A}$; (b) $R = V^2/P = 144 \Omega$.

P29 $P = 1500 \text{ W}$, $V = 120 \text{ V}$, $\alpha = 0.0045$, $\rho_0 = 5.6 \times 10^{-8} \Omega \cdot \text{m}$ & $L = 4 \text{ m}$. $R = V^2/P = 9.60$. $\rho = \rho_0 (1 + \alpha \Delta T) = 1.64 \times 10^{-7} \Omega \cdot \text{m}$, $A = \rho L/R = 6.8 \times 10^{-8} \text{ m}^2$.

P42 $\varepsilon = 3.0 \text{ V}$, $R_v = 4 \Omega$ & $R_h = 6 \Omega$: (a) The resistance of right loop, $R_a^{-1} = 1/4 + 1/16 = 5/16$, $R_a = 3.2 \Omega$, $R_{eq} = 6 + R_a + 6 = 15.2 \Omega$; (b) $I = \varepsilon/R_{eq} = 0.197 \text{ A}$.

P46 $R_{245} = 2.73 \Omega$ & $R_{362} = 1.00 \Omega$, so R_{245} & R_{362} in series $3\text{-}\Omega$ gives $R_A = 6.73 \Omega$. (a) $R_{eq} = R_A + 9 \Omega = 15.73 \Omega$; (b) $R_{39} = 2.25 \Omega$, $R_{eq} = R_A + R_{39} = 8.98 \Omega$; (c) The total current draw is $I = 12.0/8.98 = 1.34 \text{ (A)}$, $I_4 = IR_5/(R_5 + R_{24}) = 0.609 \text{ A}$

P49 $R = 5 \Omega$: (a) $R_a = (3)(5) = 15 \Omega$, $R_b = 15/4 \Omega$, $R_c = 10 + R_b = 55/4 \Omega$, $R_d = 11/3 = 3.67 \Omega$, $R_{eq} = 13.67 \Omega$; (b) $I = V/R_{eq} = 0.439 \text{ A}$; (c) $I_6 = 5I/(5 + R_c) = 0.117 \text{ A}$, $I_1 = I_6 R_d/(5 + R_a) = 0.088 \text{ (A)}$; (d) $I_2 = 0$.

P51 For junction f, $I_1 + I_2 + I_3 = 0$; For loop abcfa, $12 - 14I_2 - 3 = 0$, $I_2 = 9/14 = 0.643 \text{ (A)}$; for loop cdefc, $-6 + 10I_1 + 3 = 0$, $I_1 = 0.300 \text{ A}$. $I_3 = -(I_1 + I_2) = 0.943 \text{ A}$.

P53 $I_3 = 3 \text{ A}$. (a) For junction b, $I_2 = I_1 + I_3 \dots \textcircled{1}$. For loop abefa, $-3I_3 - 6I_2 + 9 = 0$, $6I_2 = 9 - 9 = 0$. From $\textcircled{1}$, $I_1 = -I_3 = -3.0 \text{ A}$; (b) For loop bcdeb, $-\varepsilon + 4I_1 + 6I_2 = 0$, $\varepsilon = 4I_1 = -12.0 \text{ V}$; (c) $V_4 = 4I_1 = 12.0 \text{ V}$.

P55 (a) For junction d, $I_1 + I_2 + I_3 = 0$, or $I_2 = -I_1 - I_3 \dots \textcircled{1}$; For loop abcda, $-20I_1 + 6 - 3 + 20I_2 = 0 \dots \textcircled{2}$. For loop dcfd, $-20I_2 + 3 - 8 + 15I_3 = 0 \dots \textcircled{3}$. Substitute $\textcircled{1}$ into $\textcircled{2}$ and $\textcircled{3}$, we have $40I_1 + 20I_3 = 3$ and $4I_1 + 7I_3 = 1$. Therefore, $I_3 = 0.140 \text{ A}$, $I_1 = 0.005 \text{ A}$, and $I_2 = -0.145 \text{ A}$; (b) $V_6 = 6I_3 = 0.84 \text{ V}$, $V_8 = 8I_1 = 0.04 \text{ V}$, $V_9 = 9I_3 = 1.26 \text{ V}$, $V_{12} = 12I_1 = 0.06 \text{ V}$, $V_{20} = 20I_2 = -2.9 \text{ V}$.

P63 $P_i = 1200 + 60 + 600 = 1860 \text{ (W)}$, $I_i = P_i/V = 15.5 \text{ A}$. $P_f = P_i + 40.0 = 1900 \text{ W}$, $I_f = 15.83 \text{ A}$. So the rating of the fuse is between 15.5 A and 15.8 A .